

Oct - Nov. - 2015

204-Digital Computer Organization

BCA Sem-2

Total Marks: 70

code: 2917

Time: 2.5 Hours

- Q - 1** Answer the following
- (A) What is Gate? Explain any three gates with truth table, Graphical symbol and Boolean function 07
- (B) Which gate is known as Universal Gate? Explain Universal Gates in detail 07
- OR**
- Q - 1** Answer the following
- (A) Explain De Morgan's Theorem in detail 07
- (B) Obtain Simplify Expression and Draw Circuit : $F(A,B,C) = \sum (0,1,2,3,7)$ 07
- Q - 2** Answer the following
- (A) What is Combinational Circuit? Explain 8 * 3 Encoder. 07
- (B) Explain 6 bit Comparator. 07
- OR**
- Q - 2** Answer the following
- (A) What is IC Chip? Explain types of IC chip in detail. 07
- (B) What is the use of Multiplexer? Explain 1 bit - 4 line multiplexer. 07
- Q - 3** Answer the following
- (A) What is Arithmetic Circuit? Explain Half Adder in detail 07
- (B) Explain Shift Left and Shift Right operation using 1 bit shifter 07
- OR**
- Q - 3** Answer the following
- (A) What is Subtractor? Explain Full Subtractor in detail. 07
- (B) Explain 4 bit Binary Adder in detail 07
- Q - 4** Answer the following
- (A) Explain type of RAM and ROM. Differentiate Volatile and Non Volatile Memory 07
- (B) Define Sequential Circuit. Explain Clocked RS Flip Flop 07
- OR**
- Q - 4** Answer the following
- (A) Explain D and JK Flip Flop 07
- (B) Explain Shift Register in detail. 07
- Q - 5** Answer the following
- (A) Explain General Microprocessor Chip 07
- (B) Explain Bus Clicking in detail 07
- OR**
- Q - 5** Answer the following
- (A) Explain Bus Arbitration in detail 07
- (B) Explain ISA and USB Bus. 07