

Code: 20219

Oct - 2017
B.Sc. (I.T.) Semester -2

Principle of Digital Electronics

Time: 2:30 Hours

Total Marks: 70

- Q-1(A) What is Gates? Explain types of Gates. [07]
Q-1(B) Discuss Boolean algebra with truth table. [07]
OR
Q-1(A) Prepare logical circuit from the following. [07]
 $F(A,B,C) = A + (B \bullet C) \cdot (A' + B')$
Q-1(B) State and prove De-Morgan's theorems. [07]

Q-2(A) Prepare truth table from the following. [07]
 $F(A,B,C) = (A+B) + (B \bullet C')$
Q-2(B) Explain POS in detail with example. [07]
OR
Q-2(A) Write a note on Universal Gates. [07]
Q-2(B) Explain SOP in detail with example. [07]

Q-3(A) Explain encoder and decoder in detail. [07]
Q-3(B) Discuss in detail: De Multiplexer. [07]
OR
Q-3(A) Write a detail note on Comparator. [07]
Q-3(B) Discuss in detail: Multiplexer. [07]

Q-4(A) Discuss in detail: Shifter. [07]
Q-4(B) Differentiate: (1) Half Adder – Full Adder [07]
(2) Half Subtractor– Full Subtractor.
OR
Q-4(A) Explain Binary Adder. [07]
Q-4(B) Explain Half Subtractor [07]

Q-5(A) Define flip flop. Explain JK flip flop in detail. [07]
Q-5(B) Define latches. Explain D-flip flop. [07]
OR
Q-5(A) Write a detail note on Registers. [07]
Q-5(B) Explain Asynchronous Counter. [07]
-