

10 DEC 2020

B.Sc. Sem V (PHYSICS)

Paper: 503

Title : Digital Electronics and 'C' Programming

Q:1 What is called logic gates ? give truth table of NOR gate having three inputs. Explain working of NOR gate circuit designed with diode and transistor. Explain it with only transistor. [14]

OR

Q:1 [a] Explain working of transistor based AND gate with its truth table and symbol. [07]

[b] Explain Full adder [07]

Q:2 Write Boolean expression, reduce it using mapping and implement in NOR logic: $F = m(0, 1, 4, 5, 6, 7, 11, 12, 15)$ using SOP method ? [14]

OR

Q:2 [a] Reduce the following Boolean expression [07]

$$(i) Y = \overline{A} + \overline{AB} + \overline{A+BC}$$

$$(ii) Y = \overline{A+AB} + \overline{A+AB} C$$

[b] Without reducing draw logic circuit using OR/AND/NOT gates [07]

$$(i) Y = \overline{ABC} + \overline{A+BC}$$

$$(ii) Y = (A + \overline{B} + \overline{C}) (\overline{BC})$$

Q:3 Find out Final Value of following Statement. [14]

int i = 5, j = 5, k = 7;

float a = 3.5, b = 5.5, c = 2.5;

(a) $a = b - i / j + c / j$

(b) $a = (b - i) / (j + c) / j$

(c) $a = b - ((i + j) / (k + i)) * c$

(d) $a = b - i + j / k + i * c$

(e) $a = b + 1 \% 1 + c$

(f) $a = (b + 1) \% (1 + c)$

OR

Q:3(A) Write a program in C language to find a volume of Cylinder of radius R and length L. [07]

Q:3(B) Write a program in C language to find $5p^2+2p+8$. [07]

Q:4 Write a program in C language to pick largest number of three numbers [14]

OR

Q:4(A) Flow chart to pick the smallest number of a set of three numbers. [07]

Q:4(B) write a program for following pattern using for loop. [07]

1

1 2

1 2 3

1 2 3 4

નોંધ:

- પ્રશ્નપત્રનો સમય ૧.૩૦ કલાકનો રહેશે.
- પ્રશ્નપત્રમાં ૪ પ્રશ્નોમાંથી કોઈ પણ ત્રણ પ્રશ્નોના જવાબ આપવાનો રહેશે.
- દરેક પ્રશ્નના ગુણ એકસરખા (૧૪ માર્કના) રહેશે. પ્રશ્નપત્ર કુલ ૪૨ માર્કસ નું રહેશે.