

B.Sc. Sem V (PHYSICS)

April 2016

Paper

:504

Title : Digital Electronics and Solid state devices

Code : 4297

Total : 70 marks

Time : 2.30h

Q:1 [a] What is called logic circuit? Write its truth table for three inputs NOR gate and Explain diode based circuit. [7]

[b] What is OR gate? Explain it diode based circuit. [7]

OR

Q:1 [a] What is universal gate? Explain NOR gate as universal gate with necessary block diagram. [8]

[b] Explain AND gate with transistor circuit. [6]

Q:2 Write Boolean expression, reduce it using mapping and implement in NOR logic:  $F = m(0,2,5,12,13,14,15)$  using SOP method [14]

OR

Q:2 Write Boolean expression, reduce it using mapping and implement in NOR logic:  $F = m(0,2,4,6,7,9,10,13,14,15)$  using POS method. [14]

Q:3 [a] Reduce the following Boolean expression. [12]

[1]  $\overline{(\overline{A}B + ABC)} (\overline{A}B\overline{C})$

[2]  $(A + \overline{BC}) (\overline{A}B + C)$

[3]  $(\overline{A} + \overline{BC}) (\overline{A}B\overline{C})$

[4]  $\overline{A + \overline{A} + BC} (A + \overline{BC})$

[b] Find designated value of  $\overline{A}BC$ ,  $A\overline{B}C$ ,  $ABC$ ,  $\overline{A}\overline{B}\overline{C}$  [02]

Q:3 [a] Without reducing covert following Boolean expression in to NOT/AND and OR logic. [12]

[1]  $\overline{ABC} + \overline{A}BC$

[2]  $(A + \overline{BC}) (\overline{A} + BC)$

[3]  $(\overline{A} + \overline{B} + \overline{C}) (A + B + C)$

[4]  $(A + B) (\overline{A} + \overline{B})$

[b] Write Boolean expression for the  $f(3,5,7)$  [02]

Q:4 [a] Without reducing convert the following expression to AND,OR and NOT logic. Then convert it in NOR logic circuit (two INPUT) Mention number of gates used. [10]

[1]  $(A + \overline{B + C})(\overline{A}B + C)$

[2]  $(A + \overline{B}C)(\overline{A}B + C)$

[b] Write application of LED. [04]

OR

Q:4 [a] What is DIAC ? Describe its construction, characteristic and operation with necessary circuit diagram. [08]

[b] How a Bipolar transistor can be used as ac and dc switch? [06]

Q:5 [a] Explain full adder with block diagram. [6]

[b] What is IC? Explain classification of IC's by function briefly. [8]

OR

Q:5 [a] Write short note on diode as an ac switch. [8]

[b] explain photo diode. [6]