

B.Sc. Sem. V (PHYSICS)

Paper :504

Title : Digital Electronics and Solid state devices

Code : 4297

NOV 2014

Time- 2-30

- Que.1 [a] What is universal gate? Explain NAND gate as an universal gate with necessary block diagram. [08]
- [b] Explain AND gate with transistor circuit. [06]
- OR
- Que.1 [a] What is called logic circuit? Explain diode based OR gate. [07]
- [b] What is NOT gate? Explain it as transistor circuit. [07]
- Que.2 Write Boolean expression, reduce it using mapping and implement in NOR logic: [14]  
 $F = m(2,4,6,8,10,13,14,15)$  using SOP method
- OR
- Que.2 Write Boolean expression, reduce it using mapping and implement in NOR logic: [14]  
 $F = m(2,4,6,7,12,13,14,15)$  using POS method
- Que.3 [a] Find the minterms for the following and also state their designation [12]
- [1]  $A + BC$
- [2]  $AB + ACD$
- [3]  $AB + C$
- [4]  $ABC + CD$
- [b] Find designated value of  $\overline{WX} Y \overline{Z}$  [02]
- OR
- Que.3 [a] Reduce the following expressions to the simplest form and implement in AND/OR/invert logic. [12]
- [1]  $A + \overline{AB} + AB$
- [2]  $\overline{AB} + \overline{AB} + AB + \overline{AB}$
- [3]  $\overline{ABD} + \overline{ABD} + \overline{BD}$
- [4]  $(AB + C)(AB + D)$
- [b] Write De Morgan's theorem and verify it with truth table. [02]
- Que.4 [a] Without reducing convert the following expression to AND, OR and NOT logic. [10]  
Then convert it in NAND logic circuit (two INPUT) Mention number of gates used.
- [1]  $A + B + AB$
- [2]  $(A + (A + \overline{B} + C))(\overline{ABC})$
- [b] Write application of LED. [04]

OR

Que.4[a]      What is DIAC ? Describe its construction, characteristic and operation with necessary circuit diagram.      [08]

[b]      How a Bipolar transistor can be used as ac and dc switch?      [06]

Que.5[a] Explain full adder with block diagram.      [06]

[b]      What is IC? Explain classification of IC's by function briefly.      [08]

OR

Que.5[a]      Write short note on diode as an ac switch.      [08]

[b]      Explain photo diode.      [06]