

OCT. / NOV. - 2015

P.G.D.C.A. Semester – 1

Paper – 103: Logical Organization of Computer

Time: 3 Hours

code: 25703

Total Marks: 100

Q.1 Convert the following: [20]

- a. $(23.85)_{10} = (?)_2$
- b. $(E8D6)_{16} = (?)_8$
- c. $(11111010)_2 + (10000111)_2 = (?)_2$
- d. $(123.746)_{10} = (?)_8$

OR

Q.1 Convert the following: [20]

- a. $(27)_{10} = (?)_2$
- b. $(396)_{10} = (?)_8$
- c. $(1001)_2 = (?)_{16}$
- d. $(1011101)_2 = (?)_{16}$

Q.2 Answer the following questions: [20]

- a. Explain : Instruction Execution Cycle
- b. What is the difference between serial and parallel instruction execution?
- c. Explain the Block diagram of Computer in detail
- d. Write a short note on ASCII

OR

Q.2 Answer the following questions: [20]

- a. Differentiate between Main Memory & Secondary Memory
- b. Explain the types of I/O devices.
- c. Draw Circuit Diagram of Encoder.
- d. Explain the concept of CPU Organization in detail

Q.3 Answer the following questions: [20]

- a. What do you mean by logic Gates? Explain in detail
- b. Verify the following Boolean Laws.
 - 1. $A.A=A$ 2. $A+A=1$
- c. Draw Circuit Diagram of Half Subtractor
- d. Draw Symbol of Universal Logic Gate and Give their truth-table.

OR

Q.3 Answer the following questions: [20]

- a. State two Demorgan's theorem
- b. Draw Circuit Diagram of Half Adder
- c. Explain the concept of SOP
- d. Draw circuit diagram of 3 input OR Gate using diode.

Q.4 Answer the following questions: [20]

- a. Draw circuit with truth table: $F = (A+B+C) (A'B') (A' + B')$
- b. Draw circuit of 4 bit comparator.
- c. What is the purpose of multiplexer? Draw circuit of 1 bit – 4 lines multiplexer
- d. Explain : JK Flip Flop

OR

Q.4 Answer the following questions: [20]

- a. Give the concept about half adder with gate diagram
- b. Various types of ICs
- c. Explain RS Flip Flop
- d. Explain : Buffer and Shifting .

Q.5 Answer the following questions: [20]

- a. Explain impact & nonimpact printer in detail
- b. What is memory? Explain volatile and non-volatile memory in detail.

OR

Q.5 Answer the following questions: [20]

- a. Discuss the architecture of Microprocessor.
- b. What are different addressing modes? Explain their important with example.
